

Coffer Maker FPGA

LED Interface for a Capsule Coffee Maker

Task Description

A company building capsule coffee makers has asked for a circuit that can blink an indicator LED at specific frequencies depending on what size of coffee the customer wants:



The blinking frequencies are predetermined as follows:

- Espresso (40 ml) → 1 Hz
 Lungo (110 ml) → 2 Hz
- The coffee size selection will be implemented with a single binary switch (0: espresso, 1: lungo) and there will be a second master power switch. The rest of the coffee machine is irrelevant, only the circuitry just described should be considered here. The company has agreed to an FPGA proof-of-concept implementation for now.

Moreover, to them there will be a child protection system to lock system without correct password. In that sense, specific three passwords will work with power switch so that coffee machine safely work.

Acceptance Test

The company representative will switch the power ON and simply count how many times the LED blinks within a 10-second interval with a stopwatch. Based on the provided blinking frequency requirements, the LED needs to blink 10 times within that 10-second interval for the espresso mode, and 20 times for the lungo mode.

Power switches only works when one of the passwords correctly entered. Also password switches should be open for user understand which switches open to enter correct password.



Pw#: password bit

Pw3|pw2|pw1

0	0	0	
0	0	1	
0	1	1	

Requirements

The requirements of the system are listed below, including interface (IRQ#), functional (FRQ#) and timing (TRQ#) requirements.

Interface requirements

IRQ1 – Input: 2 independent binary switches (HIGH - LOW) that maintain their state once toggled by the user. The states of these switches are called "*PWR*" and "*SEL*" in the following.

IRQ2 - Output: illumination intensity of 1 LED. This LED is called "LED" in the following.

<u>Functional requirements</u>

FRQ1 - Read *PWR* and manipulate the state of an LED blinking routine with it. Specifically, the blinking routine should start when *PWR* = HIGH, and stop when *PWR* = LOW.

FRQ2 - The LED blinking routine should alternate the illumination level of *LED* between its highest and lowest possible levels at specified frequencies called "FE" and "FL" in the following.

FRQ3 - Read SEL to choose between FE and FL for the LED blinking routine. Specifically, FL should be chosen when SEL = HIGH and FE when SEL = LOW.

<u>Timing requirements</u>

TRQ1 - The LED blinking routine should have FE = 1 Hz and FL = 2 Hz with 50% duty cycle.

TRQ2 - Counter count at 49999998 for blink cycle.

Implementation

For using VHDL code vivado used and basys3 board helps to implement it. Clock is set to 10 period so 10 ns is the period of the basys3.



I redesign switches such as:

- -- sw0: for power on and off
- -- sw1: for espresso on and lungo off
- -- sw2: most significant bit pw3
- -- sw3: second most pw2
- -- sw4: least significant bit pw1

Leds are designed for reflect which switches open, espresso or lungo and blinks for show hertz.

- --led0: Blinks to show hertz of system.
- --led1: Espresso or lungo led.
- --led2: most significant bit led led.
- --led3: second most significant bit led.
- --led4: least significant bit led.

```
30 ## LEDs
31 set_property -dict { PACKAGE_PIN U16 IOSTANDARD LVCMOS33 } [get_ports {led[0]}]
32 set_property -dict { PACKAGE_PIN E19 IOSTANDARD LVCMOS33 } [get_ports {led[1]}]
33 set_property -dict { PACKAGE_PIN U19 IOSTANDARD LVCMOS33 } [get_ports {led[2]}]
34 set_property -dict { PACKAGE_PIN V19 IOSTANDARD LVCMOS33 } [get_ports {led[3]}]
35 set_property -dict { PACKAGE_PIN W18 IOSTANDARD LVCMOS33 } [get_ports {led[4]}]
```


Creating a counter variable to 5 million and count each clock helps to reach frequency goal. However, lungo has more frequency so I count twice at each clock. That means it get 2 Hertz blink value. Without an external counter that gives more efficient solution to this problem.

I use 5 switches to represent inputs, that helps to get my input and process. Therefore I have 5 leds to indicate password (3 of leds),type of coffee(1 of leds), frequency of led(1 of the leds). Using std_logic_vector helps to more clear code. If statements helps me to decide power on and one of the password correct and then it check espresso or lungo and it blinks according to that values.



```
library IEEE;
     use IEEE.STD_LOGIC_1164.ALL;
     entity coffeemaker is
Port ( clk : in STD_LOGIC;
    led : out STD_LOGIC_Vector(4 downto 0) ;
    sv : in STD_LOGIC_Vector (4 downto 0)
     end coffeemaker:
       sw0 for power on and off
sw1 for espress on and lungo off
sw2 most significant bit pw3
sw3 second most pw2
sw4 least significant bit pw1
passwords: "000" "001" "011"
     -- passwords: "000" "001" "011" architecture Behavioral of coffeemaker is
       signal pulse : std_logic := '0';
signal count : integer range 0 to 99999999 := 0;
     begin
      process(clk, sw)
begin
        if sw(0) = '0' or not ((sw(2) = '0') and sw(3) = '0' and sw(4) = '0') or (sw(2) = '0') and sw(3) = '0' and sw(4) = '1') or (sw(2) = '0') and sw(3) = '1' and sw(4) = '1') ) then
        pulse <= '0';
elsif clk'event and clk = '1' then</pre>
         --99999999
Signal count . Integer range o co 55555555 .- o,
    begin
φ
        process(clk, sw)
        begin
φ
           if sw(0) = '0' or not ((sw(2) = '0') and sw(3) = '0' and sw(4) = '0'
           or (sw(2) = '0' \text{ and } sw(3) = '0' \text{ and } sw(4) = '1') \text{ or } (sw(2) = '0' \text{ and } sw(3) = '1' \text{ and } sw(4) = '1') ) then
                  pulse <= '0';
            elsif clk'event and clk = 'l' then
             --99999999
\Diamond
              if count >= 49999999 then
                  count <= 0;
                 pulse <= not pulse;
               elsif sw(1) = '0' or (count=49999998 ) then
                 count <= count + 1;
               elsif sw(1)='1' and not(count=49999998) then
                  count <= count+2;
\Diamond
               end if:
           end if;
\Diamond
        end process;
        led(4 downto 1) <= sw(4 downto 1);</pre>
        led(0) <= pulse;</pre>
end Behavioral;
```

 After completing code I run synthesis and get project elaborated design. This is the project schematic:



Utilization and usage of devices are:



Resource	Estimation	Available	Utilization %
LUT	17	20800	0.08
FF	27	41600	0.06
IO	11	106	10.38
BUFG	1	32	3.13

After getting synthesis design, I get implementation utilization and usage devices table:

Resource	Utilization	Available	Utilization %
LUT	16	20800	0.08
FF	27	41600	0.06
Ю	11	106	10.38
BUFG	1	32	3.13

Verification

The timing constraints in this project are very loose so we don't need complicated verification. The acceptance test itself is satisfactory.

References

https://github.com/sonebu/elec305-lab1-example/tree/main